

(4 pnts) Name/Surname:

ID:


EE 210 – Introduction to Electrical Engineering – Midterm 2

May 12, 2010

Duration: 120 min, Closed book and notes. Calculators are allowed.

Illegible answers will not be graded.

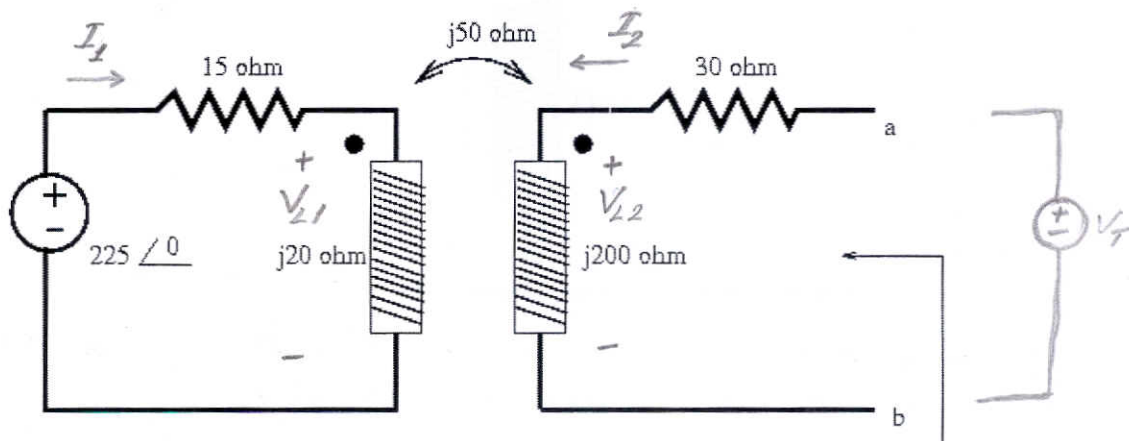1. (24pnts) Find the Thevenin equivalent circuit in phasor domain for terminals a-b.



open circuit:

$$I_2 = 0$$

$$V_{22} = V_{Th} = j50 I_1$$

$$225 = 15 I_1 + j20 I_1 + j50 I_2$$

$$I_1 = \frac{225}{15 + j20}$$

$$V_{Th} = j50 \frac{225}{15 + j20} \cdot \frac{15 - j20}{15 - j20} = \frac{225e3 + j168750}{625} = 360 + j270$$

Remove the voltage source and apply V_T to terminals a-b:

$$V_T = I_2 (30 + j200) + I_1 j50$$

$$0 = I_1 (15 + j20) + I_2 j50 \times \frac{-j50}{15 + j20}$$

$$V_T = I_2 \left[(30 + j200) + \frac{2500}{15 + j20} \right]$$

$$Z_{Th} = 30 + j200 + \frac{2500}{15 + j20} \frac{15 - j20}{15 - j20}$$

$$= 30 + j200 + 60 - j80$$

$$= 90 + j120$$

o.c. V_{Th} 12 \rightarrow 8
s.c. Z_{Th} or i_{sc} 12 \rightarrow 8


Computation error - 4

$I_2 = 0$ in o.c. missed - 6

$$V_{Th} = 360 + j270$$

$$Z_{Th} = 90 + j120$$

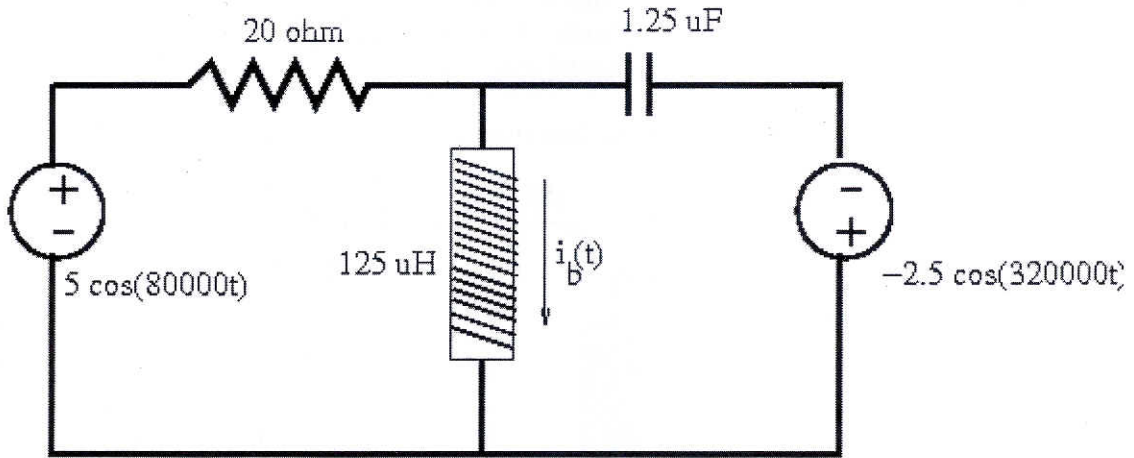2. (24pts) Find the steady state expression for $i_b(t)$.




Since the 2 voltage sources operate at different frequencies, we need to use the superposition principle:

ω	$125 \mu\text{H}$	$1.25 \mu\text{F}$
80k	$j10$	$\frac{1}{j0.1} = -j10$

Superposition principle in phasor domain 12pts
Solutio. 6+6 pts.

320k	$j40$	$\frac{1}{j0.4} = -j2.5$
---------------	-------	--------------------------

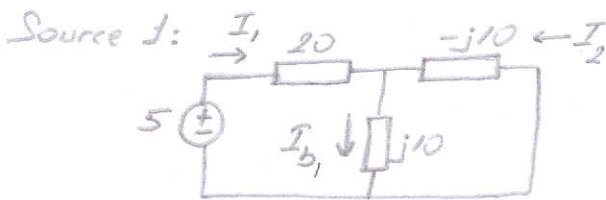


$$5 = I_1(20 + j10) + I_2 j10 \quad I_{b1} = I_1 + I_2$$

$$0 = I_2(-j10 + j10) + I_1 j10$$

$$\Rightarrow I_1 = 0 \Rightarrow I_2 = \frac{5}{j10} = -j0.5$$

$$\Rightarrow I_{b1} = -j0.5 \Rightarrow i_{b1}(t) = \text{Re}\{-j0.5 e^{j80000t}\}$$

$$= 0.5 \cos(80000t - \frac{\pi}{2})$$

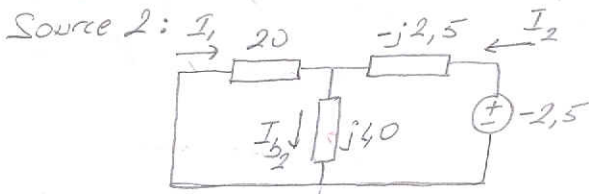

$$-2.5 = I_2 j37.5 + I_1 j40 \quad I_{b2} = I_1 + I_2$$

$$0 = I_1(20 + j40) + I_2(-j2.5)$$

$$-2.5 = I_2(80 + j37.5)$$

$$I_2 = \frac{-2.5}{80 + j37.5} \Rightarrow I_1 = -I_2 j2 = \frac{j5}{80 + j37.5}$$

$$I_{b2} = \frac{-2.5 + j5}{80 + j37.5} \cdot \frac{80 - j37.5}{80 - j37.5} = -0.0016 + j0.0633$$

$$i_b(t) = 0.5 \cos(80000t - \frac{\pi}{2}) + 0.0633 \cos(320000t + 0.508\pi)$$

$$i_{b2}(t) = \text{Re}\{(-0.0016 + j0.0633) e^{j320000t}\}$$

$$= \text{Re}\{0.0633 e^{j0.508\pi} e^{j320000t}\}$$

$$= 0.0633 \cos(320000t + 0.508\pi)$$


$0.5^{0.508\pi} = 1.5961$

3. (6+6+12pts) The switch in the circuit shown has been in position A for a long time.

a. $V_a(0^+) = ?$

b. $\left. \frac{dV_a(t)}{dt} \right|_{t=0^+} = ?$

c. $V_a(t) = ?$

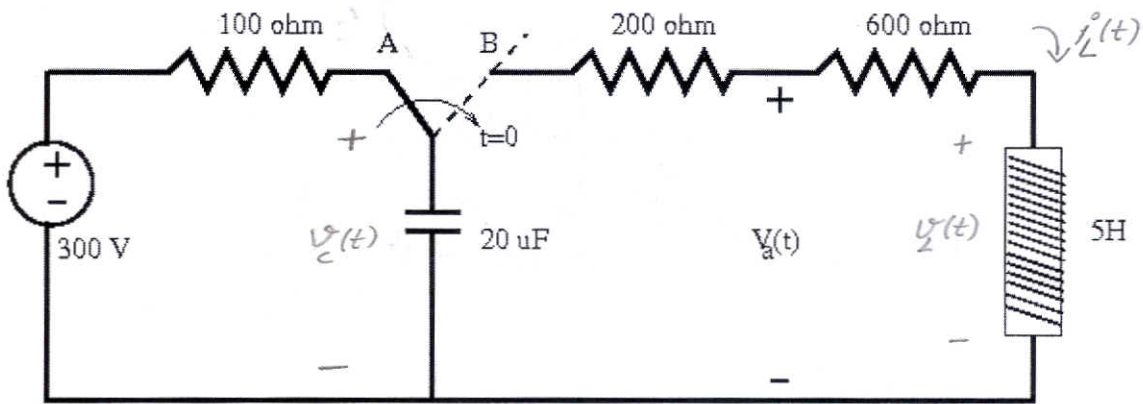

Continuous circuit parameters


a) $V_c(0^-) = V_c(0^+) = 300 \text{ V}$ (Capacitor o.c. in switch position A) $-i_L = C \frac{dV_c}{dt}; V_c$
 $i_L(0^-) = i_L(0^+) = 0 \text{ A} \Rightarrow V_a(0^+) = V_c(0^+) = 300 \text{ V}$ $V_L = L \frac{di_L}{dt}; i_L$
 & $V_L(0^+) = 300 \text{ V}$

b) $V_a = V_c - 200 i_L$
 $\frac{dV_a}{dt} = \frac{dV_c}{dt} - 200 \frac{di_L}{dt} = \frac{-i_L}{C} - 200 \frac{V_L}{L} \Rightarrow \left. \frac{dV_a}{dt} \right|_{t=0^+} = \frac{-i_L(0^+)}{C} - 200 \frac{V_L(0^+)}{L}$
 $= 0 - 200 \frac{300}{5} = -12000$

c) KVL for switch position B:
 $V_c = 800 i_L + 5 \frac{di_L}{dt} \Rightarrow \frac{dV_c}{dt} = 800 \frac{di_L}{dt} + 5 \frac{d^2 i_L}{dt^2} \Rightarrow \frac{-i_L}{C} = 800 \frac{di_L}{dt} + 5 \frac{d^2 i_L}{dt^2}$
 $\Rightarrow i_L'' + 160 i_L' + 10000 i_L = 0 \quad \alpha^2 - \omega_0^2 = -3600 < 0 \text{ underdamped.}$
 $\omega_d \approx 60$ soln form or ODE: 6
 $i_L(t) = e^{-80t} (\beta_1 \cos \omega_d t + \beta_2 \sin \omega_d t)$ type of soln: 6 (damping)
numeric result: 5 (bonus)

$V_a(t) = 600 i_L(t) + 5 i_L'(t)$
 $= 600 e^{-80t} (\beta_1 \cos \omega_d t + \beta_2 \sin \omega_d t) + 5(-80) e^{-80t} () + 5 e^{-80t} (-\beta_1 \omega_d \sin \omega_d t + \beta_2 \omega_d \cos \omega_d t)$
 $= 200 e^{-80t} () + 5 e^{-80t} (-\beta_1 \omega_d \sin \omega_d t + \beta_2 \omega_d \cos \omega_d t)$
 $300 = 600 \beta_1 - 400 \beta_2 + 5 \beta_2 \omega_d = 200 \beta_1 + 300 \beta_2$
 $-12000 = -36000 \beta_1 - 12000 \beta_2$
 $\beta_1 = 0$
 $\beta_2 = 1$

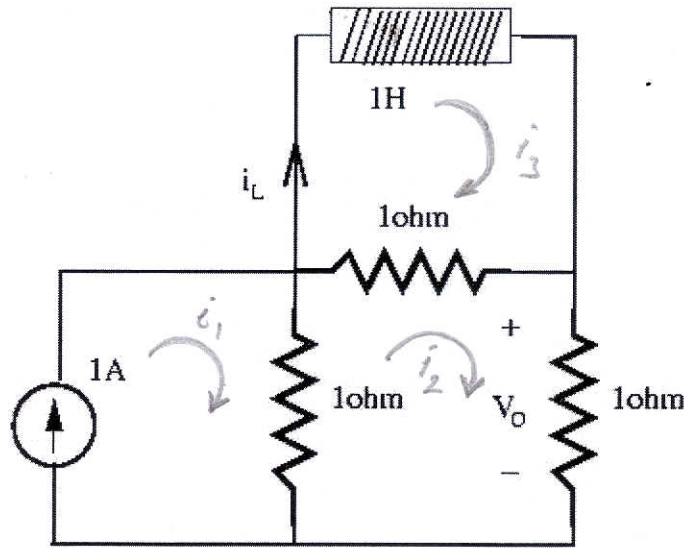4. (24pts) For the following circuit, determine $V_O(t)$ for $t > 0$, given $i_L(0) = 2A$.



$$i_1 = 1A$$

$$i_2 - i_1 + i_2 - i_3 + i_2 = 0 = 3i_2 - i_1 - i_3 = 3i_2 - 1 - i_3$$

$$\frac{di_3}{dt} + i_3 - i_2 = 0$$

$$\Rightarrow 3\left(i_2 + \frac{di_3}{dt}\right) - 1 - i_3 = 0$$

$$3 \frac{di_3}{dt} + 2i_3 = 1$$

$$\frac{di_3}{dt} = \frac{-2}{3} \left(i_3 - \frac{1}{3}\right)$$

$$\frac{di_3}{i_3 - \frac{1}{3}} = \frac{-2}{3} dt$$

$$\ln \frac{i_3(t) - \frac{1}{3}}{i_3(0) - \frac{1}{3}} = \frac{-2}{3} t$$

$$i_3(t) - \frac{1}{3} = \left(i_3(0) - \frac{1}{3}\right) e^{-\frac{2}{3}t}$$

$$i_3(t) = \frac{1}{3} + \frac{5}{3} e^{-\frac{2}{3}t}$$

$$\Rightarrow i_2 = V_O(t) = \frac{1 + i_3(t)}{3} = \frac{1}{3} \left(\frac{4}{3} + \frac{5}{3} e^{-\frac{2}{3}t} \right) = \frac{4}{9} + \frac{5}{9} e^{-\frac{2}{3}t}$$

Correct $\ln\left(\frac{1}{2}\right) \rightarrow e^{-\frac{2}{3}t}$ (10)