

Q) We have a 100mV, 1mA d'Arsonval meter movement


a) Design an Ammeter circuit by using this d'Arsonval movement with full-scale current of 50mA.

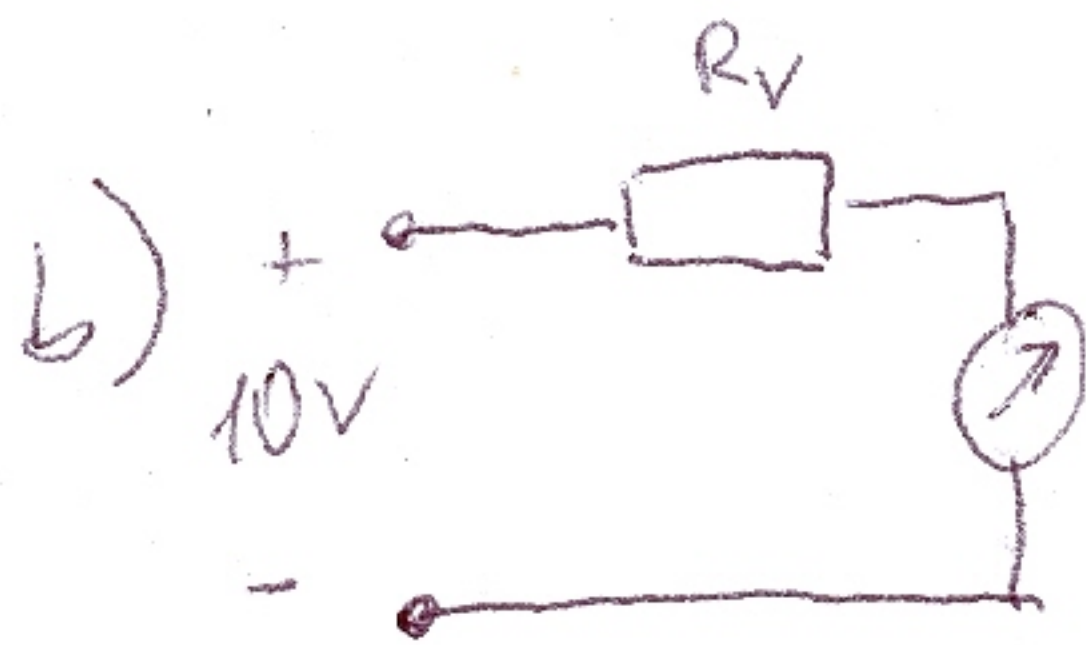b) Design a Voltmeter circuit by using it with full-scale voltage of 10V.



1mA \rightarrow coil for 1mA \Rightarrow voltage drop = 100mV
 49mA \rightarrow R_A

$$49 \times 10^{-3} R_A = 100 \times 10^{-3} \Rightarrow \underline{R_A \approx 2.04 \Omega}$$



$$R_{d'Arms} = \frac{100mV}{1mA} = 100 \Omega$$

$$100 \times 10^{-3} V = \frac{100}{100 + R_V} \times 10V \Rightarrow R_V = \frac{1000 - 100}{100 \times 10^{-3}}$$

$$\Rightarrow \underline{R_V = 9.9 k\Omega}$$